

Project 1


Professor Umer Cheema

Design of a 16-bit Arithmetic Logic Unit


Sean Atangan 655409356

10/17/2021


Block Diagram

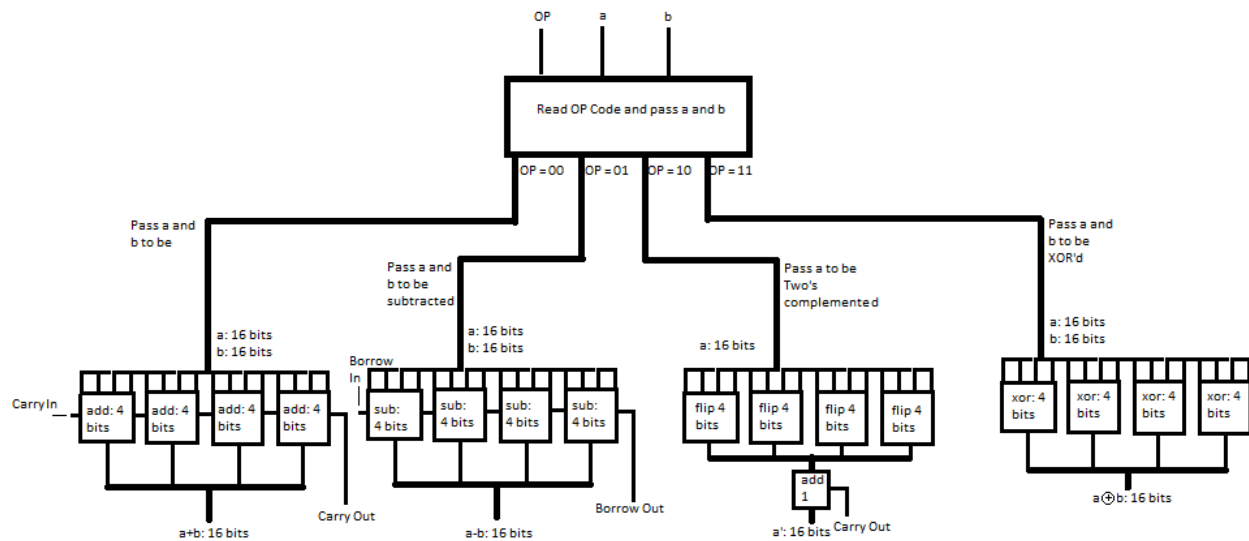


Sixteen Bit ALU

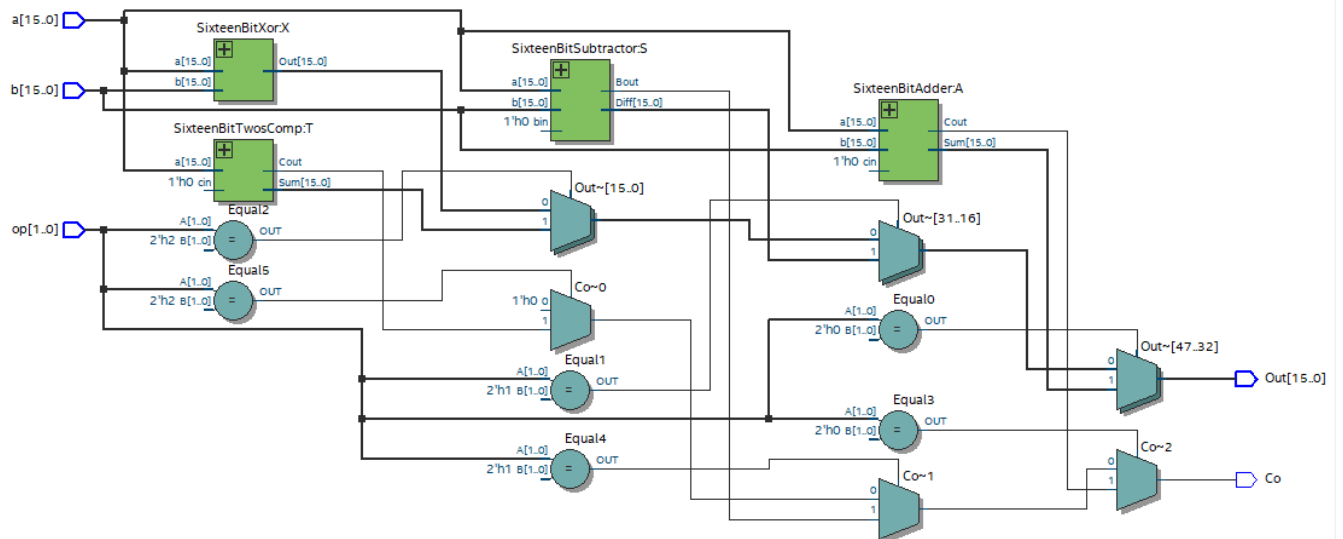


Sixteen Bit Adder

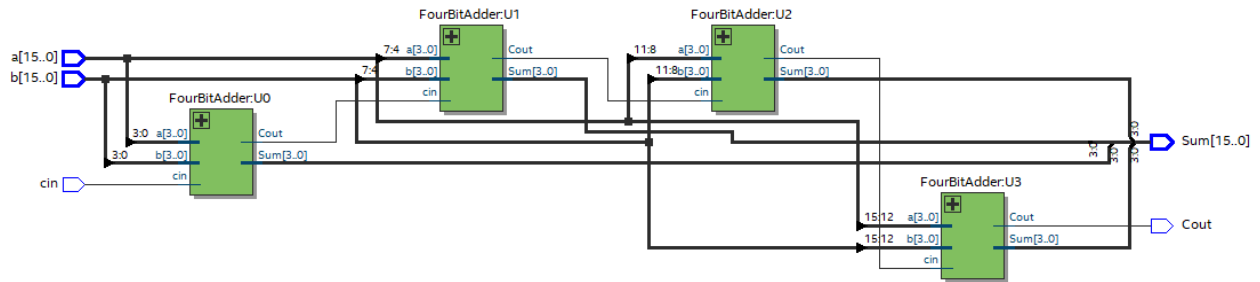

Four Bit Adder

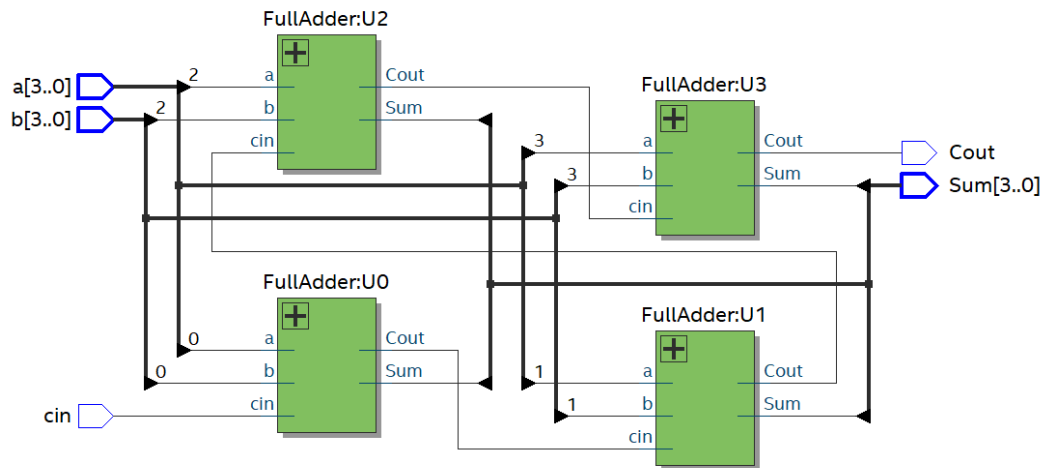

Full Adder

 


Minimization Logic for Full Adder:


Truth Table

A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

K-Maps

 


$$S = A \text{ or } B \text{ or } C$$

 


$$\begin{aligned} C_{out} &= AB + BC + AC \\ &= (A \text{ or } B)C + AB \end{aligned}$$


Sixteen Bit Subtractor

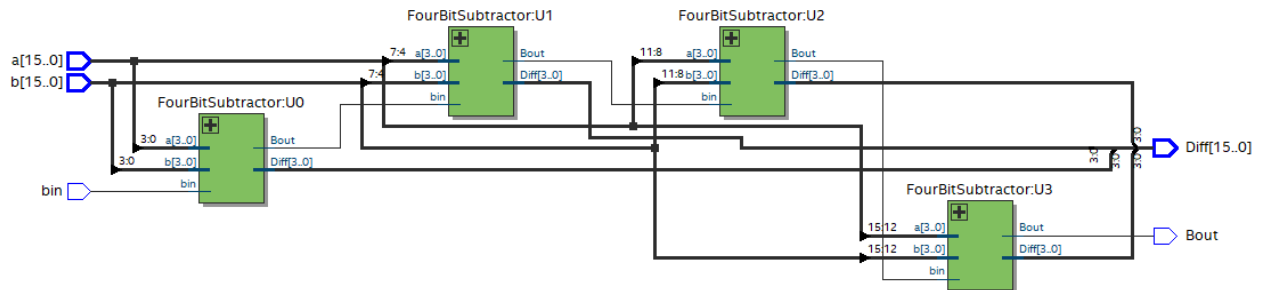

Four Bit Subtractor

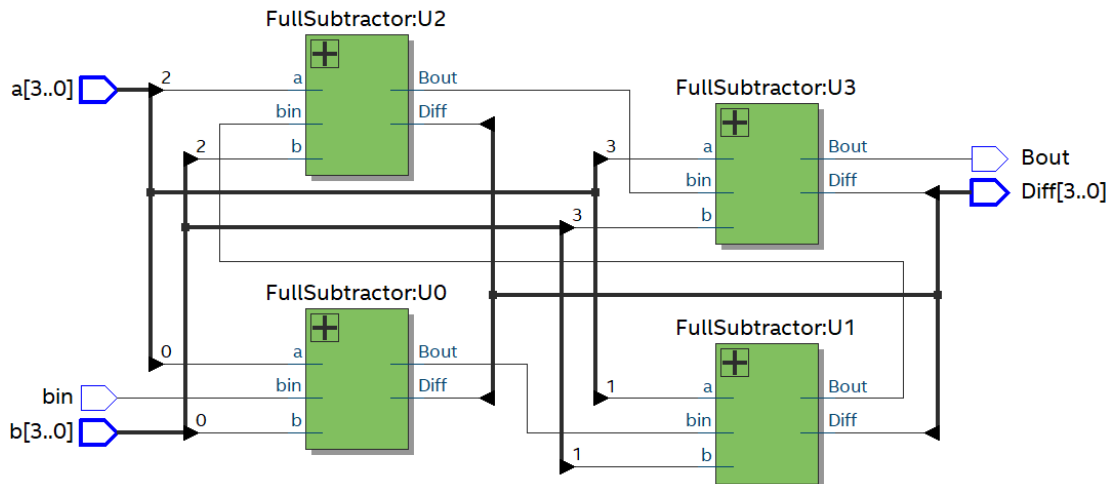

Full Subtractor

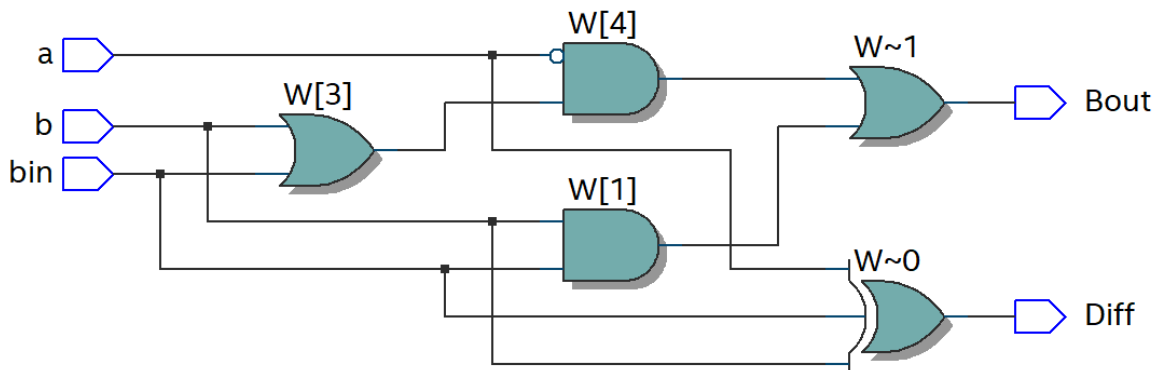

Minimization Logic for Full Subtractor:

Truth Table

A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

K-Maps


		D	
		0	1
AB	00	0	1
	01	1	0
	11	0	1
	10	1	0

$$\text{Diff} = A \text{ or } B \text{ or } D$$


		D	
		0	1
AB	00	0	1
	01	1	1
	11	0	1
	10	0	0

$$\begin{aligned} \text{Bout} &= A'D + BD + A'B \\ &= A'(B+D) + BD \end{aligned}$$


Sixteen Bit Two's Complement

 


Sixteen Bit Inverter

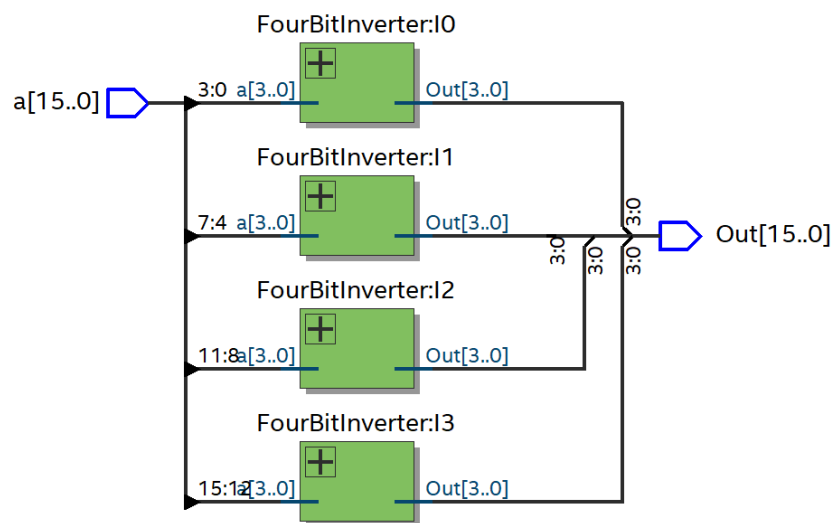


Four Bit Inverter

 

Sixteen Bit XOR

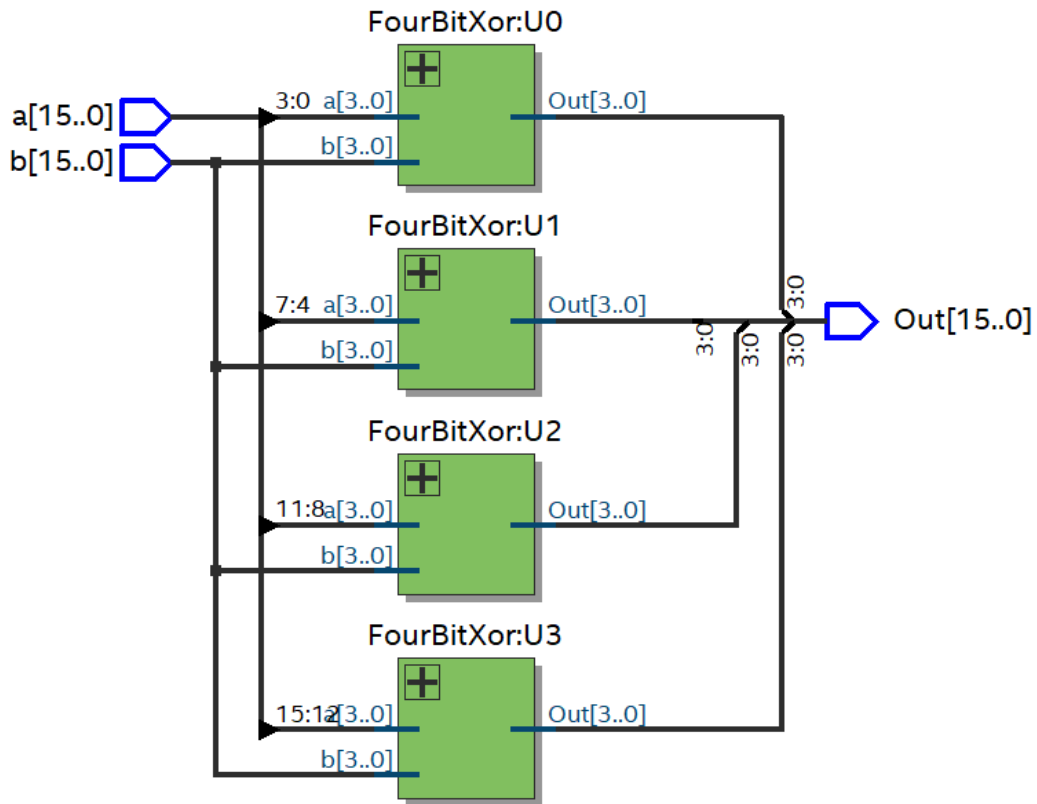

Four Bit XOR

 

Testing:

Testing 16-bit adder for general output and carry bit: **Passed**

[illegible]

```

186 initial begin
187
188     a = 16'd0;
189     b = 16'd0;
190     op = 2'd0;
191
192     #100
193
194     a = 16'b1111111111111111;
195     b = 16'd1;
196
197     #100
198
199     a = 16'd1;
200     b = 16'd1;
201
202     #100
203
204     a = 16'd2;
205     b = 16'd2;
206
207     #100
208
209     a = 16'd3;
210     b = 16'd3;
211     #100
212
213     a = 16'd4;
214     b = 16'd4;

```

Testing 16-bit subtracter for general output and borrow bit: **Passed**

[illegible]

```

186 initial begin
187
188     a = 16'd0;
189     b = 16'd0;
190     op = 2'd1;
191
192     #100
193
194     a = 16'b0000000000000000;
195     b = 16'd1;
196
197     #100
198
199     a = 16'd8;
200     b = 16'd1;
201
202     #100
203
204     a = 16'd8;
205     b = 16'd2;
206
207     #100
208
209     a = 16'd256;
210     b = 16'd1;
211     #100
212
213     a = 16'd256;
214     b = 16'd2;

```

Testing 16-bit Two's Complement for general output and carry bit: **Passed**

	Msgs												
/ALU_tb/op	10	10											
/ALU_tb/a	0000000000000000	0000000000000000			1111111111111111		0000000011111111		0101010101010101		1010101010101010		
/ALU_tb/b	0000000000000000	0000000000000000											
/ALU_tb/Out	0000000000000000	0000000000000000			0000000000000001		1111111100000001		1010101010101011		0101010101010110		
/ALU_tb/Co	St1												

```

186 initial begin
187
188     a = 16'd0;
189     b = 16'd0;
190     op = 2'd2;
191
192     #100
193
194     a = 16'b0000000000000000;
195     b = 16'd0;
196
197     #100
198
199     a = 16'b1111111111111111;
200     b = 16'd0;
201
202     #100
203
204     a = 16'b0000000011111111;
205     b = 16'd0;
206
207     #100
208
209     a = 16'b0101010101010101;
210     b = 16'd0;
211     #100
212
213     a = 16'b1010101010101010;
214     b = 16'd0;
215

```

Testing 16-bit XOR for general output: **Passed**

File	Address	Disassembly	Comment
/ALU_tb/op	11		
/ALU_tb/a	0000000000000000	0000000000000000	1111111111111111
/ALU_tb/b	0101010101010101	0101010101010101	0001000100010001
/ALU_tb/Out	0101010101010101	0000000000000000	1111111111111111
/ALU_tb/Co	HZ		

```

186      initial begin
187
188          a = 16'd0;
189          b = 16'd0;
190          op = 2'd3;
191
192          #100
193
194          a = 16'b0000000000000000;
195          b = 16'b0101010101010101;
196
197          #100
198
199          a = 16'b1111111111111111;
200          b = 16'b0001000100010001;
201
202          #100
203
204          a = 16'b1111111111111111;
205          b = 16'b1111111111111111;
206
207          #100
208
209          a = 16'b0000000000000000;
210          b = 16'b0000000000000000;
211          #100
212
213          a = 16'b1010101010101010;
214          b = 16'b0;
215

```

Conclusion:

This 16-bit ALU was designed to perform four different operations on two 16-bit operands a and b . Among receiving a 2-bit OP code of 00, a combination of 2x1 MUXs allow for the ALU to select the 16-bit Adder component, which comprises of four, 4-bit Adders. Each 4-bit Adder also contains four Full-Adder components. The 16-bit Adder was designed with abstraction in mind to further minimize hardware complexity, as well as improve the efficiency of the circuit by method of divide-and-conquer. Similarly, abstraction was used for the 16-bit Subtractor, 16-bit Two's Complement, and 16-Bit XOR for the same reasons. Each sub-component of the 16-bit ALU perform carry in and carry out functionality- save for the 16-Bit XOR that of which the output carry bit is don't care. All sub-components were tested for correct outputs to ensure the integrity of the 16-bit ALU's hardware logic.

Verilog Code:

```
// Author: Sean Atangan
// Professor Umer Cheema
// University Of Illinois at Chicago
// ECE 465
// This program is a design for a 16-bit ALU with
// Addition, Subtraction, Two's Complement, and XOR functionality

// 16 Bit ALU
module ALU (op, a, b, Out, Co);
    input [15:0] a;
    input [15:0] b;
    input [1:0] op;
    output [15: 0] Out;
    output Co;
    wire [15:0] Add;
    wire [15:0] Sub;
    wire [15:0] Two;
    wire [15:0] Xor;
    wire [15:0] W;
    wire [3:0] C;
    wire cin = 1'd0;
    SixteenBitAdder A(.a(a[15:0]), .b(b[15:0]), .cin(cin) , .Cout(C[0]), .Sum(Add[15:0]));
    SixteenBitSubtractor S(.a(a[15:0]), .b(b[15:0]), .bin(cin), .Bout(C[1]), .Diff(Sub[15:0]));
    SixteenBitTwosComp T(.a(a[15:0]), .cin(cin), .Cout(C[2]), .Sum(Two[15:0]));
    SixteenBitXor X(.a(a[15:0]), .b(b[15:0]), .Out(Xor[15:0]));

    // Output Bits
    assign Out[15:0] = ({op[1],op[0]} == 2'b00) ? Add[15:0] : // If OP code is 00, MUX
    chooses the 16bitAdder
    ({op[1],op[0]} == 2'b01) ? Sub[15:0] : // If OP code is 01, MUX
    chooses the 16bitSubtractor
    ({op[1],op[0]} == 2'b10) ? Two[15:0] : // If OP code is 10, MUX
    chooses the 16bitTwosComp
```

```

        ({op[1],op[0]} == 2'b11) ? Xor[15:0]: 1'bx ;           // If OP code is 11, MUX
chooses the 16bitXOR

                                                                    // Carry Out

        assign Co = ({op[1],op[0]} == 2'b00) ? C[0] :           // If OP code is 00, MUX chooses the
16bitAdder

        ({op[1],op[0]} == 2'b01) ? C[1] :                       // If OP code is 01, MUX chooses the
16bitSubtractor

        ({op[1],op[0]} == 2'b10) ? C[2] :                       // If OP
code is 10, MUX chooses the 16bitTwosComp

        ({op[1],op[0]} == 2'b11) ? C[3]: 1'bx ;               // If OP code is 11, MUX
chooses the 16bitXOR

endmodule

```

```

// Add

```

```

*****

```

```

module SixteenBitAdder (a, b, cin, Cout, Sum);

    input [15:0] a;
    input [15:0] b;
    input cin;
    output [15:0] Sum;
    output Cout;
    wire [15:0] Z;
    wire [3:0] W;

    FourBitAdder FA0(.a(a[3:0]), .b(b[3:0]), .cin(cin), .Cout(W[0]), .Sum(Z[3:0]));
    FourBitAdder FA1(.a(a[7:4]), .b(b[7:4]), .cin(W[0]), .Cout(W[1]), .Sum(Z[7:4]));
    FourBitAdder FA2(.a(a[11:8]), .b(b[11:8]), .cin(W[1]), .Cout(W[2]), .Sum(Z[11:8]));
    FourBitAdder FA3(.a(a[15:12]), .b(b[15:12]), .cin(W[2]), .Cout(W[3]), .Sum(Z[15:12]));

    assign Sum[15:0] = Z[15:0];
    assign Cout = W[3];

endmodule

module FourBitAdder (a, b, cin, Cout, Sum);

    input [3:0] a;

```

```

    input [3:0] b;
    input cin;
    output [3:0] Sum;
    output Cout;
    wire [3:0] Z;
    wire [3:0] W;
    FullAdder Fv0(.a(a[0]), .b(b[0]), .cin(cin), .Cout(W[0]), .Sum(Z[0]));
    FullAdder Fv1(.a(a[1]), .b(b[1]), .cin(W[0]), .Cout(W[1]), .Sum(Z[1]));
    FullAdder Fv2(.a(a[2]), .b(b[2]), .cin(W[1]), .Cout(W[2]), .Sum(Z[2]));
    FullAdder Fv3(.a(a[3]), .b(b[3]), .cin(W[2]), .Cout(W[3]), .Sum(Z[3]));
    assign Sum[3:0] = Z[3:0];
    assign Cout = W[3];
endmodule

module FullAdder(a, b, cin, Cout, Sum);
    input a;
    input b;
    input cin;
    output Sum;
    output Cout;
    assign {Cout, Sum} = a + b + cin;
endmodule

// Subtract
*****

module SixteenBitSubtractor (a, b, bin, Bout, Diff);
    input [15:0] a;
    input [15:0] b;
    input bin;
    output [15:0] Diff;
    output Bout;
    wire [15:0] Z;
    wire [3:0] W;

```



```

FourBitSubtractor FS0(.a(a[3:0]), .b(b[3:0]), .bin(bin), .Bout(W[0]), .Diff(Z[3:0]));
FourBitSubtractor FS1(.a(a[7:4]), .b(b[7:4]), .bin(W[0]), .Bout(W[1]), .Diff(Z[7:4]));
FourBitSubtractor FS2(.a(a[11:8]), .b(b[11:8]), .bin(W[1]), .Bout(W[2]), .Diff(Z[11:8]));
FourBitSubtractor FS3(.a(a[15:12]), .b(b[15:12]), .bin(W[2]), .Bout(W[3]), .Diff(Z[15:12]));
assign Diff[15:0] = Z[15:0];
assign Bout = W[3];
endmodule

module FourBitSubtractor (a, b, bin, Bout, Diff);
    input [3:0] a;
    input [3:0] b;
    input bin;
    output [3:0] Diff;
    output Bout;
    wire [3:0] Z;
    wire [3:0] W;

    FullSubtractor Fs0(.a(a[0]), .b(b[0]), .bin(bin), .Bout(W[0]), .Diff(Z[0]));
    FullSubtractor Fs1(.a(a[1]), .b(b[1]), .bin(W[0]), .Bout(W[1]), .Diff(Z[1]));
    FullSubtractor Fs2(.a(a[2]), .b(b[2]), .bin(W[1]), .Bout(W[2]), .Diff(Z[2]));
    FullSubtractor Fs3(.a(a[3]), .b(b[3]), .bin(W[2]), .Bout(W[3]), .Diff(Z[3]));

    assign Diff[3:0] = Z[3:0];
    assign Bout = W[3];
endmodule

module FullSubtractor(a, b, bin, Bout, Diff);
    input a;
    input b;
    input bin;
    output Diff;
    output Bout;
    wire[5:0]W;
    assign W[0] = a^b;
    assign W[1] = b&bin;

```

```

    assign W[2] = bin^W[0]; // Diff
    assign W[3] = b|bin;
    assign W[4] = !a&W[3];
    assign W[5] = W[1]|W[4]; //Bout
    assign Diff = W[2];
    assign Bout = W[5];
endmodule

// Two's Complement
*****

module SixteenBitTwosComp (a, cin, Cout, Sum);
    input [15:0] a;
    input cin;
    output [15:0] Sum;
    output Cout;
    wire [15:0] Z;
    wire [15:0] S;
    wire C;

    SixteenBitInverter I0(.a(a[15:0]), .Out(Z[15:0]));
    SixteenBitAdder A0(.a(Z[15:0]), .b(16'b1), .cin(cin), .Cout(C), .Sum(S[15:0]));
    assign Sum[15:0] = S[15:0];
    assign Cout = C;
endmodule

module SixteenBitInverter (a, Out);
    input [15:0] a;
    output [15:0] Out;
    wire [15:0] W;

    FourBitInverter I0 (.a(a[3:0]), .Out(W[3:0]));
    FourBitInverter I1 (.a(a[7:4]), .Out(W[7:4]));
    FourBitInverter I2 (.a(a[11:8]), .Out(W[11:8]));
    FourBitInverter I3 (.a(a[15:12]), .Out(W[15:12]));
    assign Out[15:0] = W[15:0];
endmodule

```

```

endmodule

module FourBitInverter(a, Out);
    input [3:0] a;
    output [3:0] Out;
    assign Out[0] = !a[0];
    assign Out[1] = !a[1];
    assign Out[2] = !a[2];
    assign Out[3] = !a[3];
endmodule

```

// Bitwise XOR

```

module SixteenBitXor (a, b, Out);
    input [15:0] a;
    input [15:0] b;
    output [15:0] Out;
    wire [15:0] Z;
    wire [3:0] W;
    FourBitXor FX0(.a(a[3:0]), .b(b[3:0]), .Out(Z[3:0]));
    FourBitXor FX1(.a(a[7:4]), .b(b[3:0]), .Out(Z[7:4]));
    FourBitXor FX2(.a(a[11:8]), .b(b[3:0]), .Out(Z[11:8]));
    FourBitXor FX3(.a(a[15:12]), .b(b[3:0]), .Out(Z[15:12]));
    assign Out[15:0] = Z[15:0];
endmodule

```

```

module FourBitXor (a, b, Out);
    input [3:0] a;
    input [3:0] b;
    output [3:0] Out;
    wire [3:0] Z;
    wire [3:0] W;
    wire N = 1;
    wire [3:0] A;

```

```
    xor(Out[0], a[0], b[0]);  
    xor(Out[1], a[1], b[1]);  
    xor(Out[2], a[2], b[2]);  
    xor(Out[3], a[3], b[3]);  
endmodule
```